


I Love This Book

1. Print out the template and either draw the cover of a book you love in the empty rectangle or stick in a picture of it.



2. Next, take a sheet of sugar paper, cut it in half so that it's 2cm wider than the template with the book cover. Mark in pencil on the sugar paper where the middle of the heart is on the template. This is where you'll put your LED.

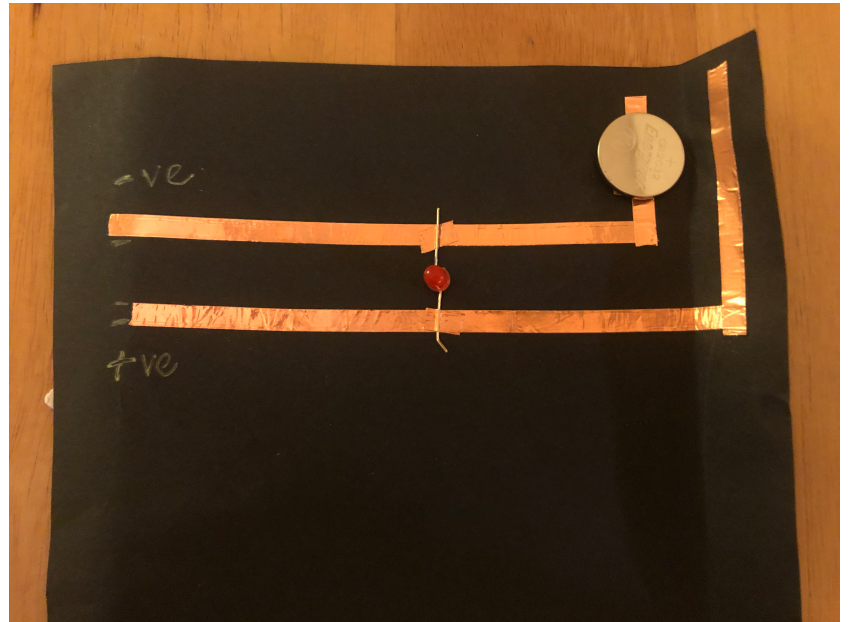3. Now make two 'L' shapes using copper tape so that the mark for the LED is in between them.
4. Attach the negative (shorter) leg of the LED to the **top L** using another bit of copper tape.
5. Attach the battery, using a loop of copper tape, so that the negative side is touching the top L.



6. Attach the positive (longer) leg of the LED to the **bottom L**
7. Fold the right hand edge of the sugar paper over so that the vertical part of the bottom L touches the battery. Your LED should light up.
8. Attach your template with book cover to the sugar paper using sellotape or glue.

9. Write "Press Here" on the top right-hand corner so that people know what to do to light the heart up.

